

# صاعق الناموس

## Outline


- 1 نظرة عامه.
- 2 الفكره الأساسيه والتطبيق.
- 3 الشرح المبسط.
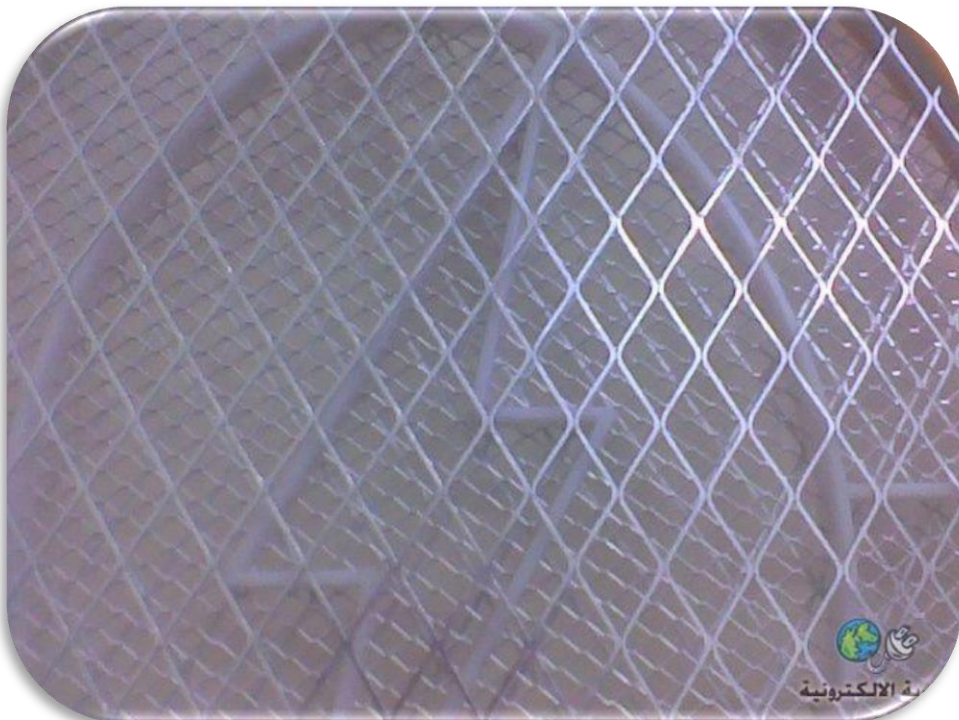
## 1-التعريف

عبارة عن دائره تنتج جهد عالي بين 2000 الى 2500 فولت بشدة تيار ضعيفه جدا ودا كفيل انه يقتل أي حشره تلمس الشبكه.



الشبكة عبارة عن شبكتين بينهم عازل يمنع تلامسهم كما بالصورة وكل شبكه عبارة عن قطب من اقطاب الخرج



## 2- الفكرة الأساسية:

تضخيم الجهد من 220V إلى 2000 أو 2500 فولت وطبعا تكبير الفولت يعني على التيار فيكون التيار ضعيف جدا ودي بتحمينا احنا لو اتكهربنا منه.



مبدأ التضخيم بطريقتين:

الطريقة القديمة: استخدام Transformer

ودي مشكلته انه غالي جدا في السعر






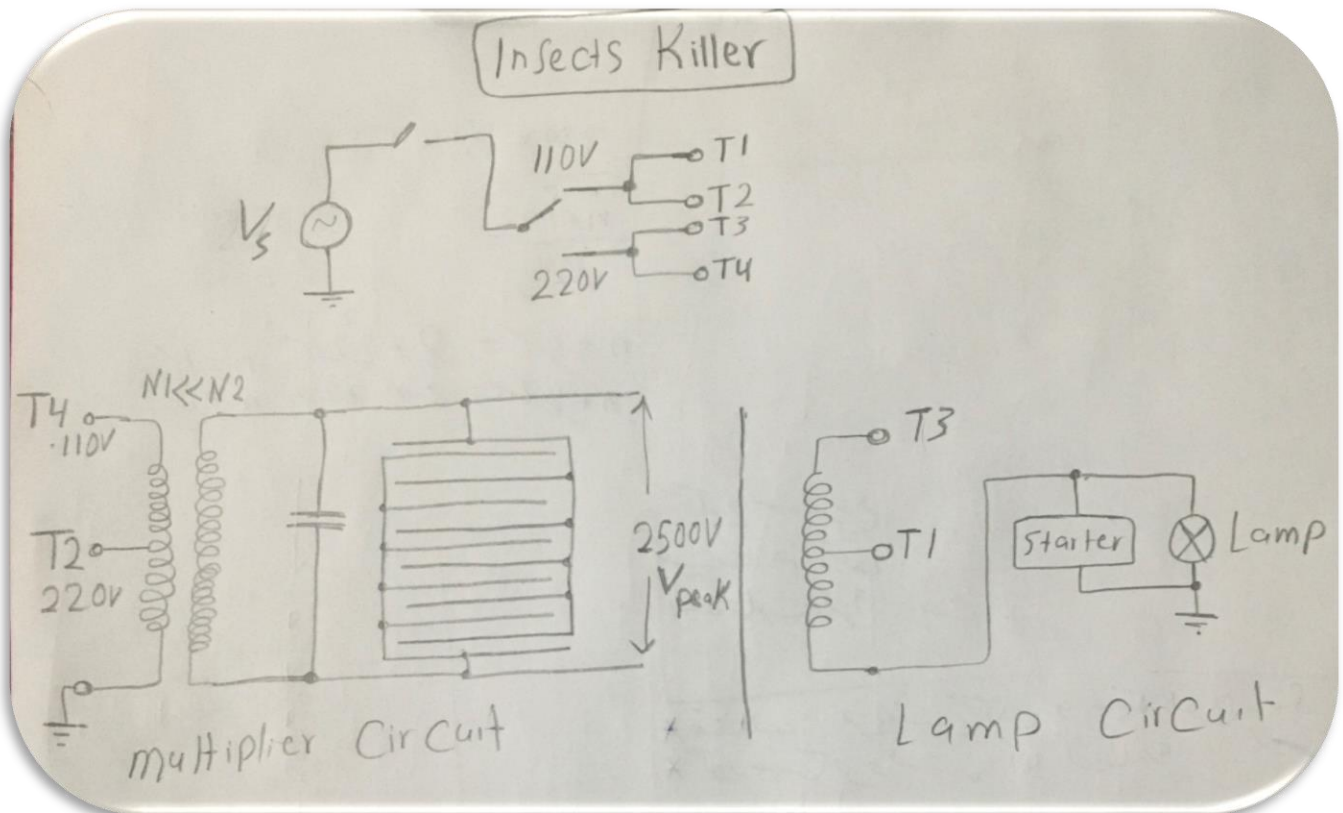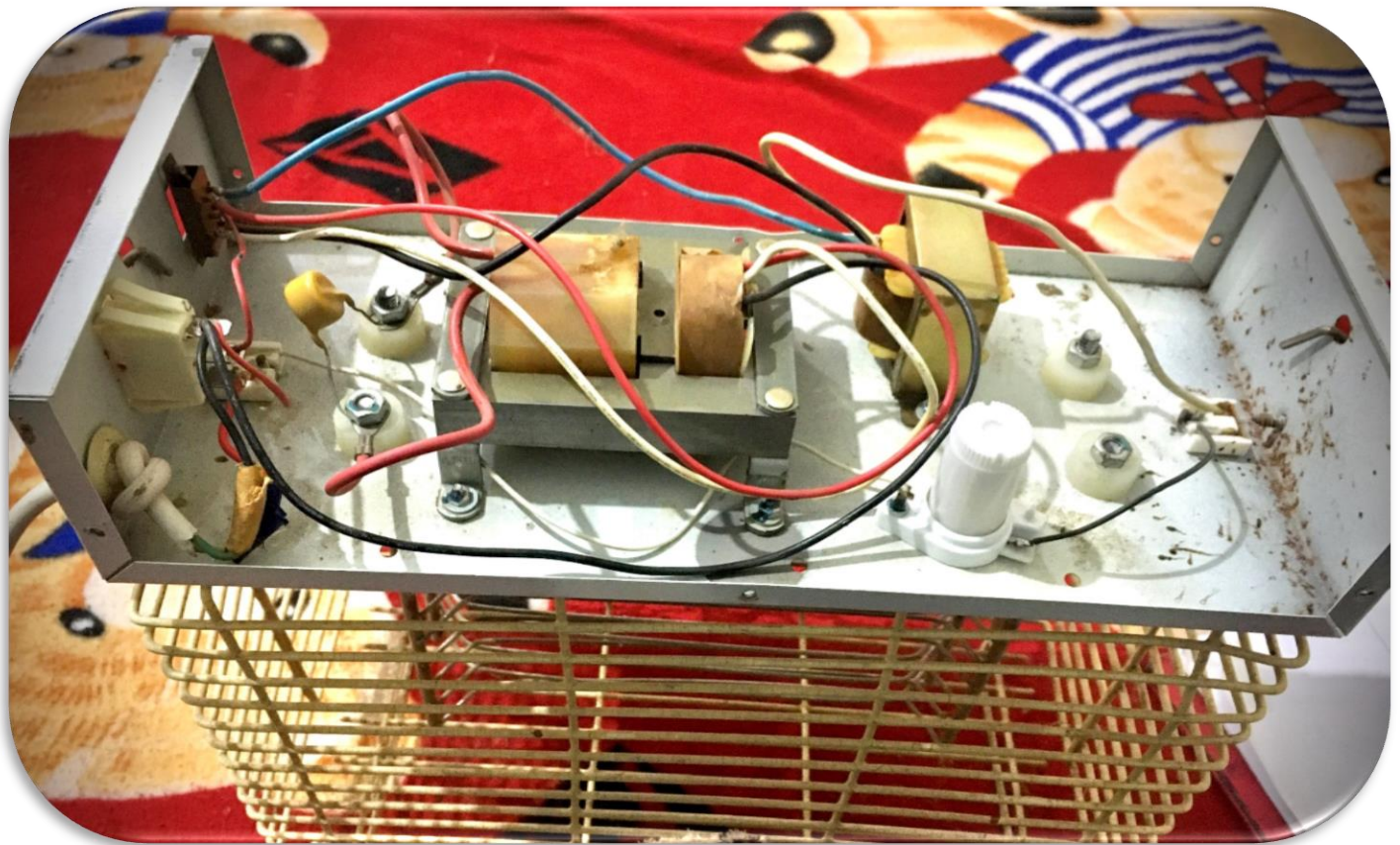
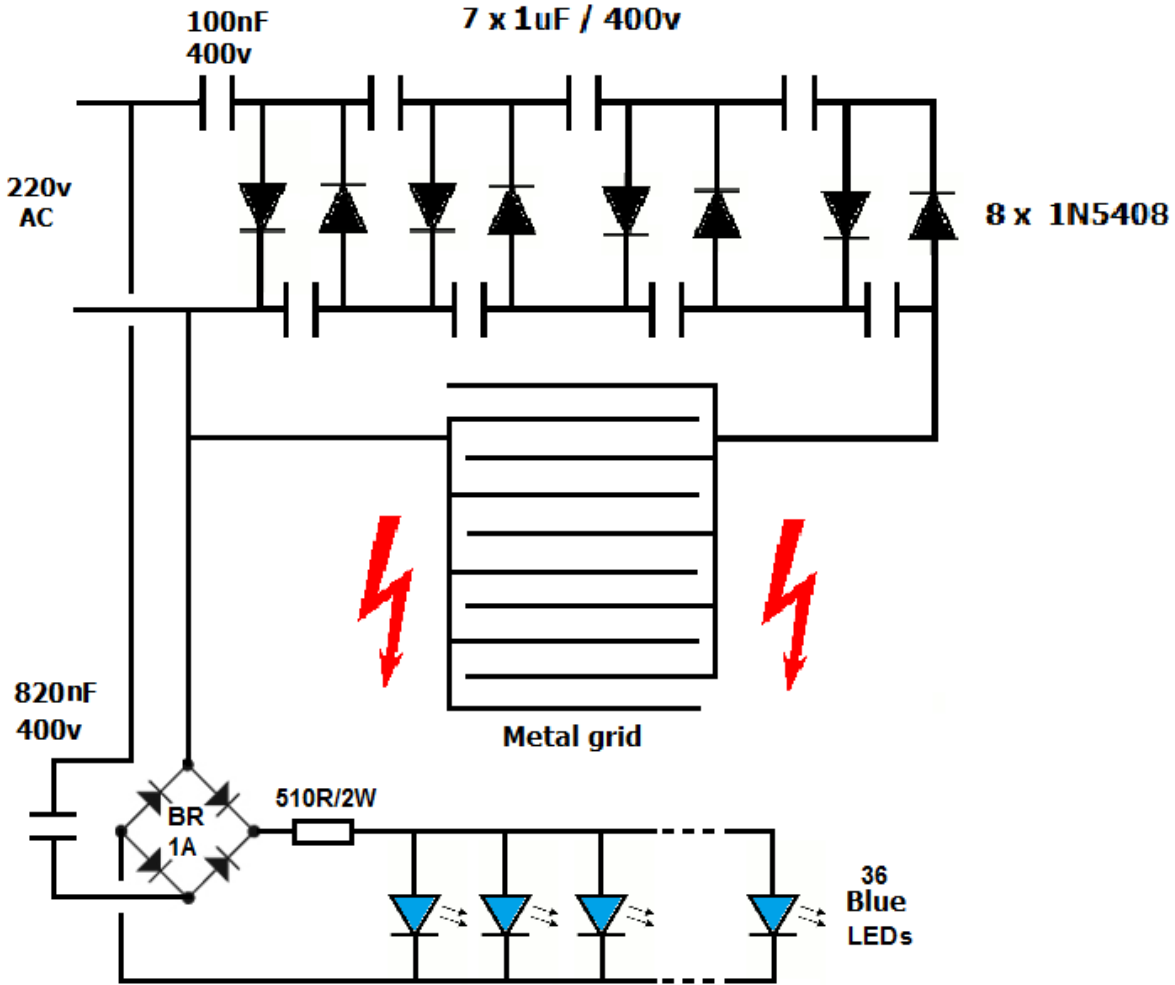
## الطريقة الحالية: استخدام دائرة Voltage Multiplier

ودي كويسه جدا من حيث التكلفة رخيصه جدا لاعتمادها على دايودات ومكثفات فقط



تعديل بسيط: المكثفات نختارها تستحمل 600 فولت لان كل مكثف يشحن  $2 * V_{peak}$  فولت ممكن هيتحرق.

الجهد الكلي = جهد المصدر ( $V_{peak}$ ) \* عدد مراحل

في الدائره السابقه 8 مراحل

$$\text{الجهد الكلي} = 8 * 220\sqrt{2} = 1760 \text{ فولت}$$

## Diode Clambers

A clamper adds a dc level to an ac voltage. **Clambers** are sometimes known as *dc restorers*. Figure 2–63 shows a diode clamper that inserts a positive dc level in the output waveform. The operation of this circuit can be seen by considering the first negative half-cycle of the input voltage. When the input voltage initially goes negative, the diode is forward-biased, allowing the capacitor to charge to near the peak of the input ( $V_{p(in)} - 0.7 \text{ V}$ ), as shown in Figure 2–63(a). Just after the negative peak, the diode is reverse-biased. This is because the cathode is held near  $V_{p(in)} - 0.7 \text{ V}$  by the charge on the capacitor. The capacitor can only discharge through the high resistance of  $R_L$ . So, from the peak of one negative half-cycle to the next, the capacitor discharges very little. The amount that is discharged, of course, depends on the value of  $R_L$ .

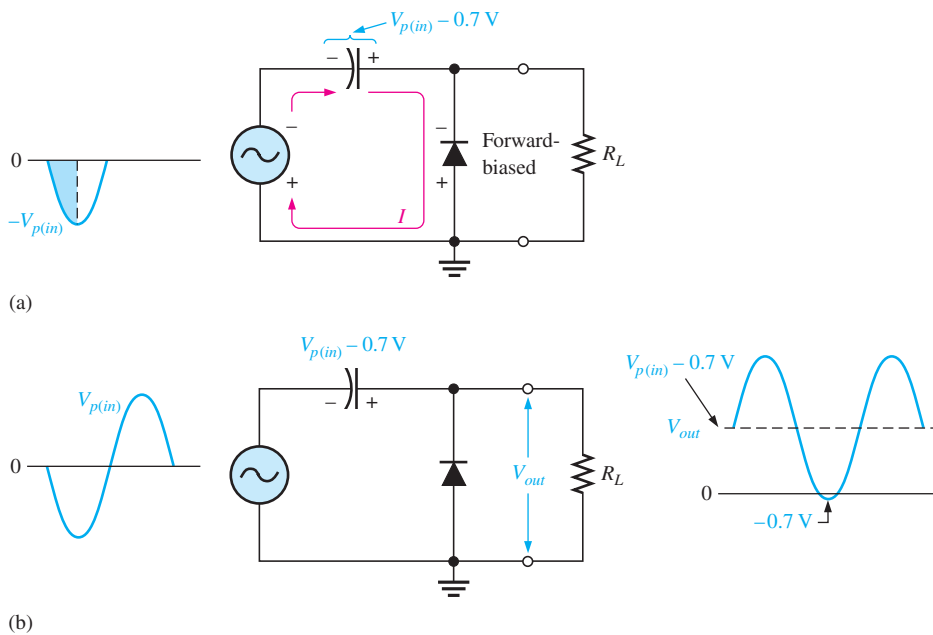


FIGURE 2–63

Positive clamper operation.

If the capacitor discharges during the period of the input wave, clamping action is affected. If the  $RC$  time constant is 100 times the period, the clamping action is excellent. An  $RC$  time constant of ten times the period will have a small amount of distortion at the ground level due to the charging current.

The net effect of the clamping action is that the capacitor retains a charge approximately equal to the peak value of the input less the diode drop. The capacitor voltage acts essentially as a battery in series with the input voltage. The dc voltage of the capacitor adds to the input voltage by superposition, as in Figure 2–63(b).

If the diode is turned around, a negative dc voltage is added to the input voltage to produce the output voltage as shown in Figure 2–64.

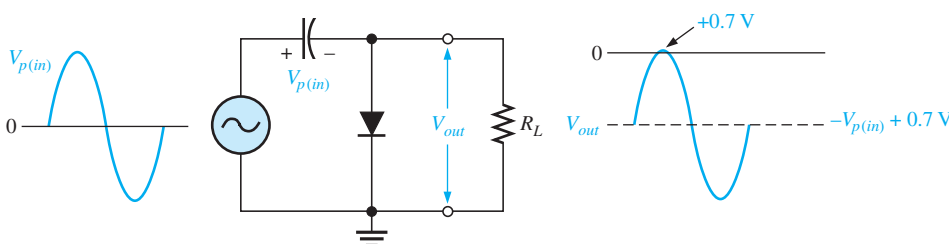



FIGURE 2–64

Negative clamper.

### EXAMPLE 2-13

What is the output voltage that you would expect to observe across  $R_L$  in the clamping circuit of Figure 2-65? Assume that  $RC$  is large enough to prevent significant capacitor discharge.

► FIGURE 2-65

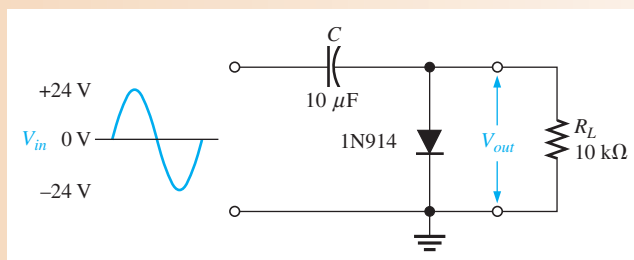


**Solution** Ideally, a negative dc value equal to the input peak less the diode drop is inserted by the clamping circuit.

$$V_{DC} \cong -(V_{p(in)} - 0.7 \text{ V}) = -(24 \text{ V} - 0.7 \text{ V}) = -23.3 \text{ V}$$

Actually, the capacitor will discharge slightly between peaks, and, as a result, the output voltage will have an average value of slightly less than that calculated above. The output waveform goes to approximately +0.7 V, as shown in Figure 2-66.

► FIGURE 2-66

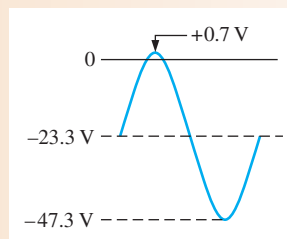Output waveform across  $R_L$  for Figure 2-65.



**Related Problem** What is the output voltage that you would observe across  $R_L$  in Figure 2-65 for  $C = 22 \mu\text{F}$  and  $R_L = 18 \text{ k}\Omega$ ?



Open the Multisim file E02-13 in the Examples folder on the companion website. For the specified input, measure the output waveform. Compare with the waveform shown in the example.

### SECTION 2-7 CHECKUP

1. Discuss how diode limiters and diode clammers differ in terms of their function.
2. What is the difference between a positive limiter and a negative limiter?
3. What is the maximum voltage across an unbiased positive silicon diode limiter during the positive alternation of the input voltage?
4. To limit the output voltage of a positive limiter to 5 V when a 10 V peak input is applied, what value must the bias voltage be?
5. What component in a clamping circuit effectively acts as a battery?

## 2-8 VOLTAGE MULTIPLIERS

Voltage multipliers use clamping action to increase peak rectified voltages without the necessity of increasing the transformer's voltage rating. Multiplication factors of two, three, and four are common. Voltage multipliers are used in high-voltage, low-current applications such as cathode-ray tubes (CRTs) and particle accelerators.

After completing this section, you should be able to

- ❑ Explain and analyze the operation of diode voltage multipliers
- ❑ Discuss voltage doublers
  - ◆ Explain the half-wave voltage doubler
  - ◆ Explain the full-wave voltage doubler
- ❑ Discuss voltage triplers
- ❑ Discuss voltage quadruplers

### Voltage Doubler


**Half-Wave Voltage Doubler** A voltage doubler is a **voltage multiplier** with a multiplication factor of two. A half-wave voltage doubler is shown in Figure 2-67. During the positive half-cycle of the secondary voltage, diode  $D_1$  is forward-biased and  $D_2$  is reverse-biased. Capacitor  $C_1$  is charged to the peak of the secondary voltage ( $V_p$ ) less the diode drop with the polarity shown in part (a). During the negative half-cycle, diode  $D_2$  is forward-biased and  $D_1$  is reverse-biased, as shown in part (b). Since  $C_1$  can't discharge, the peak voltage on  $C_1$  adds to the secondary voltage to charge  $C_2$  to approximately  $2V_p$ . Applying Kirchhoff's law around the loop as shown in part (b), the voltage across  $C_2$  is

$$V_{C1} - V_{C2} + V_p = 0$$

$$V_{C2} = V_p + V_{C1}$$

Neglecting the diode drop of  $D_2$ ,  $V_{C1} = V_p$ . Therefore,

$$V_{C2} = V_p + V_p = 2V_p$$

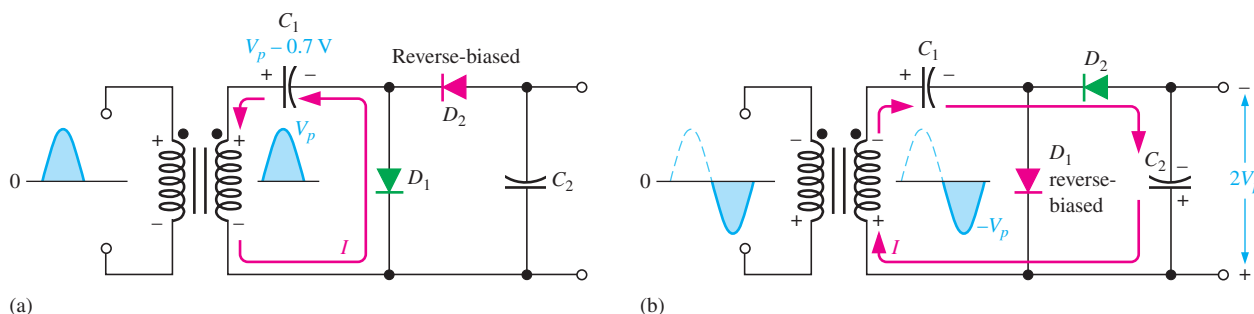


▲ FIGURE 2-67

Half-wave voltage doubler operation.  $V_p$  is the peak secondary voltage.

Under a no-load condition,  $C_2$  remains charged to approximately  $2V_p$ . If a load resistance is connected across the output,  $C_2$  discharges slightly through the load on the next positive half-cycle and is again recharged to  $2V_p$  on the following negative half-cycle. The resulting output is a half-wave, capacitor-filtered voltage. The peak inverse voltage across each diode is  $2V_p$ . If the diode were reversed, the output voltage across  $C_2$  would have the opposite polarity.



**Full-Wave Voltage Doubler** A full-wave doubler is shown in Figure 2–68. When the secondary voltage is positive,  $D_1$  is forward-biased and  $C_1$  charges to approximately  $V_p$ , as shown in part (a). During the negative half-cycle,  $D_2$  is forward-biased and  $C_2$  charges to approximately  $V_p$ , as shown in part (b). The output voltage,  $2V_p$ , is taken across the two capacitors in series.

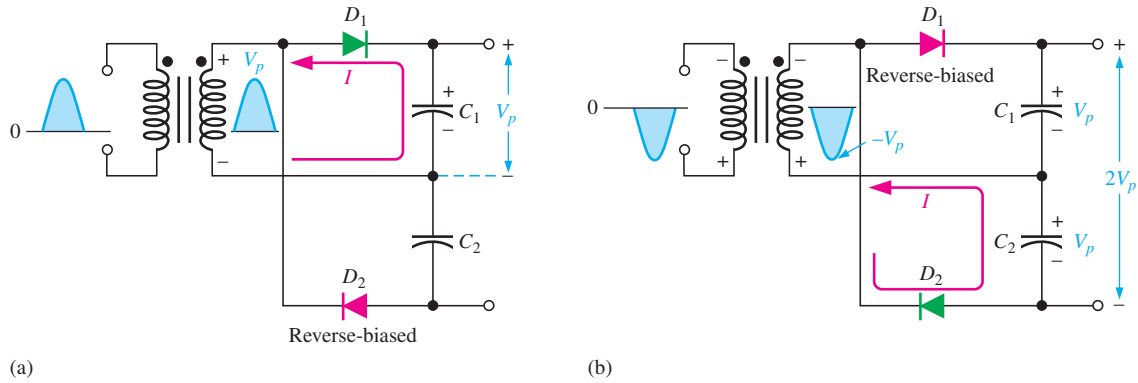

▲ FIGURE 2–68


Full-wave voltage doubler operation.

### Voltage Tripler

The addition of another diode-capacitor section to the half-wave voltage doubler creates a voltage tripler, as shown in Figure 2–69. The operation is as follows: On the positive half-cycle of the secondary voltage,  $C_1$  charges to  $V_p$  through  $D_1$ . During the negative half-cycle,  $C_2$  charges to  $2V_p$  through  $D_2$ , as described for the doubler. During the next positive half-cycle,  $C_3$  charges to  $2V_p$  through  $D_3$ . The tripler output is taken across  $C_1$  and  $C_3$ , as shown in the figure.

► FIGURE 2–69

Voltage tripler.

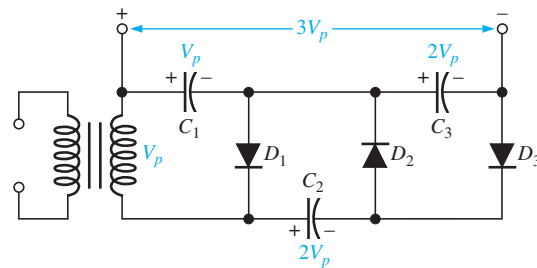


### Voltage Quadrupler

The addition of still another diode-capacitor section, as shown in Figure 2–70, produces an output four times the peak secondary voltage.  $C_4$  charges to  $2V_p$  through  $D_4$  on a negative half-cycle. The  $4V_p$  output is taken across  $C_2$  and  $C_4$ , as shown. In both the tripler and quadrupler circuits, the PIV of each diode is  $2V_p$ .

► FIGURE 2–70

Voltage quadrupler.

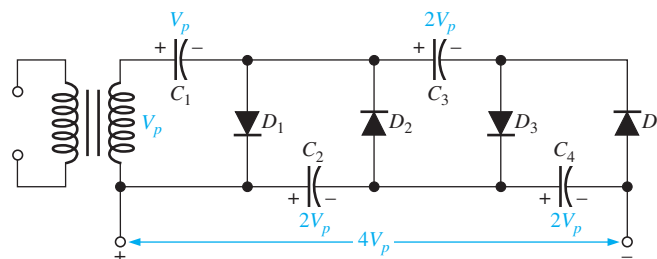

## Reference

Electronic devices (Electron version) Floyd: Diodes Applications section Chapter 2